

JEPPIAAR INSTITUTE OF TECHNOLOGY

“Self-Belief | Self Discipline | Self Respect”

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

LECTURE NOTES EE8451 – LINEAR INTEGRATED CIRCUITS AND APPLICATIONS (Regulation 2017)



**Year/Semester: II/IV EEE
2020 – 2021**

**Prepared by
Dr. S. Kamatchi
Associate Professor/ECE**

UNIT III APPLICATIONS OF OPAMP

9

Instrumentation amplifier and its applications for transducer Bridge, Log and Antilog Amplifiers- Analog multiplier & Divider, first and second order active filters, comparators, multivibrators, waveform generators, clippers, clampers, peak detector, S/H circuit, D/A converter (R-2R ladder and weighted resistor types), A/D converters using opamps.

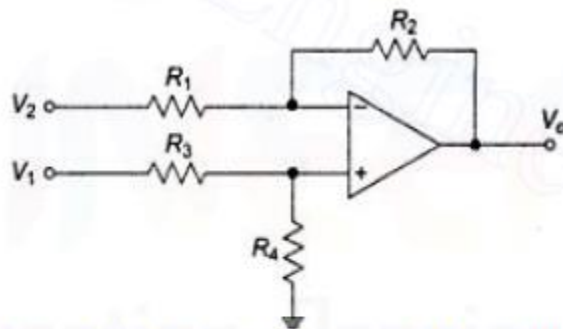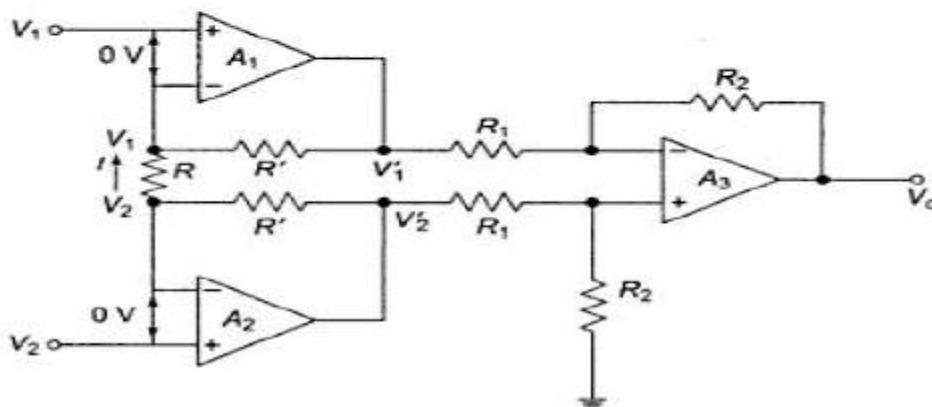Instrumentation Amplifier:**Fig. 2.18 Basic Differential Amplifier****Fig. 2.19 Instrumentation Amplifier**

Current flowing in resistor R is $I = (V_1 - V_2)/R$ and it flows through R' in the direction shown, Voltage

at non-inverting terminal op-amp A3 is $R_2 V_1' / (R_1 + R_2)$. By superposition theorem,

$$V_o = (R_2/R_1)V_1 + (1 + R_2/R_1)(R_2 V_2 / (R_1 + R_2)) = R_2/R_1 (V_1' - V_2');$$

$$V_1' = R'I + V_1 = R'/R(V_1 - V_2) + V_1$$

$$V_2' = R'I + V_2 = R'/R(V_1 - V_2) + V_2;$$

$$V_o = (R_2/R_1)[(2R'/R(V_2 - V_1) + (V_2 - V_1))] = (R_2/R_1)[(1 + 2R'/R)(V_2 - V_1)]$$

In a number of industrial and consumer applications, one is required to measure and control physical quantities. Some typical examples are measurement and control of temperature, humidity, light intensity, water flow etc. these physical quantities are usually measured with help of transducers. The output of transducer has to be amplified so that it can drive the indicator or display system. This function is performed by an instrumentation amplifier. The important features of an instrumentation amplifier are

1. High gain accuracy
2. High CMRR
3. High gain stability with low temperature coefficient
4. Low output impedance

There are specially designed op-amps such as $\mu A725$ to meet the above stated requirements of a good instrumentation amplifier. Monolithic (single chip) instrumentation amplifier are also available commercially such as AD521, AD524, AD620, AD624 by Analog Devices, LM363.XX (XX \rightarrow 10, 100, 500) by National Semiconductor and INA101, 104, 3626, 3629 by Burr Brown. In the circuit of figure 6(a), source V1 sees an input impedance = $R_3 + R_4$ (=101K) and the impedance seen by source V2 is only R_1 (1K). This low impedance may load the signal source

heavily. Therefore, high resistance buffer is used preceding each input to avoid this loading effect as shown in figure

The op-amp A1 and A2 have differential input voltage as zero. For $V_1 = V_2$, that is, under common mode condition, the voltage across R will be zero. As no current flows through R and R' the non-inverting amplifier. A1 acts as voltage follower, so its output $V_2' = V_2$. Similarly op-amp A2 acts as voltage follower having output $V_1' = V_1$. However, if $V_1 \neq V_2$, current flows in R and R' , and $(V_2' - V_1') > (V_2 - V_1)$. Therefore, this circuit has differential gain and CMRR more compared to the single opamp circuit of figure 2.10. The difference gain of this instrumentation amplifier R, however should never be made zero, as this will make the gain infinity. To avoid such a situation, in a practical circuit, a fixed resistance in series with a potentiometer is used in place of R. Figure (c) shows a differential instrumentation amplifier using Transducer Bridge. The circuit uses a resistive transducer whose resistance changes as a function of the physical quantity to be measured. The bridge is initially balanced by a dc supply voltage V_{dc} so that $V_1 = V_2$. As the physical quantity changes, the resistance R_T of the transducer also changes, causing an unbalance in the bridge ($V_1 \neq V_2$). This differential voltage now gets amplified by the three opamp differential instrumentation amplifier.

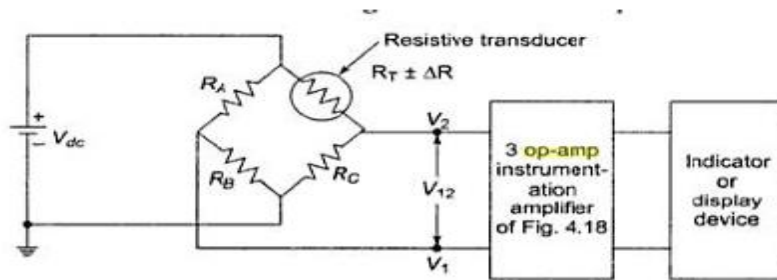


Fig.2.20 Instrumentation bridge using transducer Bridge

$$R_B(V_{dc})/(R_B+R_A) = R_C V_{dc}/(R_C+R_T)$$

Applications of instrumentation amplifier with the transducer bridge,

- temperature indicator,
- temperature controller and
- light intensity meter.

LOG AMPLIFIER:

Log Amplifier:

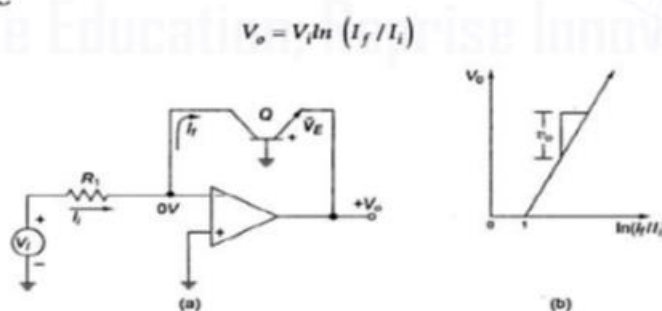


Fig 2.28 Fundamental log-amp Circuit and its characteristics

There are several applications of log and antilog amplifiers.

Antilog computation may require functions such as $\ln x$, $\log x$ or $\sin hx$.

Uses:

Direct dB display on a digital Voltmeter and Spectrum analyzer. Log-amp can also be used to compress the dynamic range of a signal. A grounded base transistor is placed in the feedback path. Since the collector is placed in the feedback path. Since the collector is held at virtual ground and the base is also grounded, the transistor's voltage-current relationship becomes that of a diode and is given by,

$$I_E = I_S [e^{\frac{qV_{BE}}{kT}} - 1] \text{ and since } I_C = I_E \text{ for a grounded base transistor } I_C = I_S e^{\frac{qV_{BE}}{kT}}$$

I_S = emitter saturation current $\approx 10^{-13}$ A

k = Boltzmann's constant

T = absolute temperature (in $^{\circ}$ K)

$$V_o = -\frac{kT}{q} \ln\left(\frac{V_i}{R_1 I_S}\right) = -\frac{kT}{q} \ln\left(\frac{V_i}{V_R}\right)$$

where $V_{ref} = R_1 I_S$

The output voltage is thus proportional to the logarithm of input voltage.

Although the circuit gives natural log (ln), one can find log10, by proper scaling

$$\text{Log}_{10} X = 0.4343 \ln X$$

The circuit has one problem. The emitter saturation current I_S varies from transistor to transistor and with temperature. Thus a stable reference voltage V_{ref} cannot be obtained. This is eliminated by the circuit given below

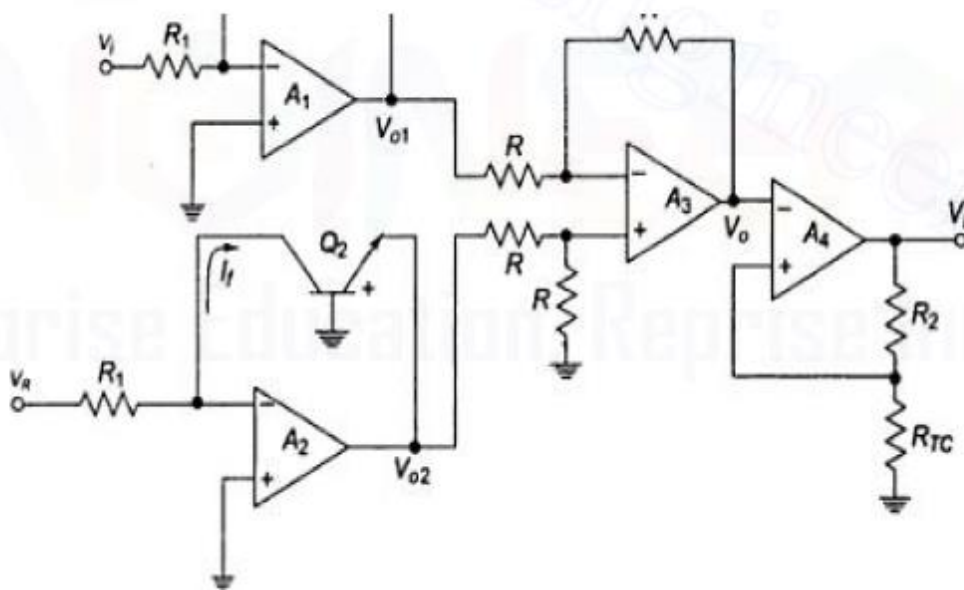


Fig. 2.29 Logarithmic amplifier with compensation of emitter saturation current

The input is applied to one log-amp, while a reference voltage is applied to one log-amp, while a reference voltage is applied to another log-amp. The two transistors are integrated close together in the same silicon wafer. This provides a close match of saturation currents and ensures good thermal tracking.

Assume $I_{S1} = I_{S2} = I_S$

Thus the reference level is now set with a single external voltage source. Its dependence on device and temperature has been removed. The voltage V_o is still dependent upon temperature and is directly proportional to T . This is compensated by the last op-amp stage A_4 which provides a non-inverting gain of $(1+R_2/R_{TC})$. Temperature compensated output voltage V_L

$$V_L = \left(1 + \frac{R_2}{R_{TC}}\right) \frac{kT}{q} \ln\left(\frac{V_i}{V_R}\right)$$

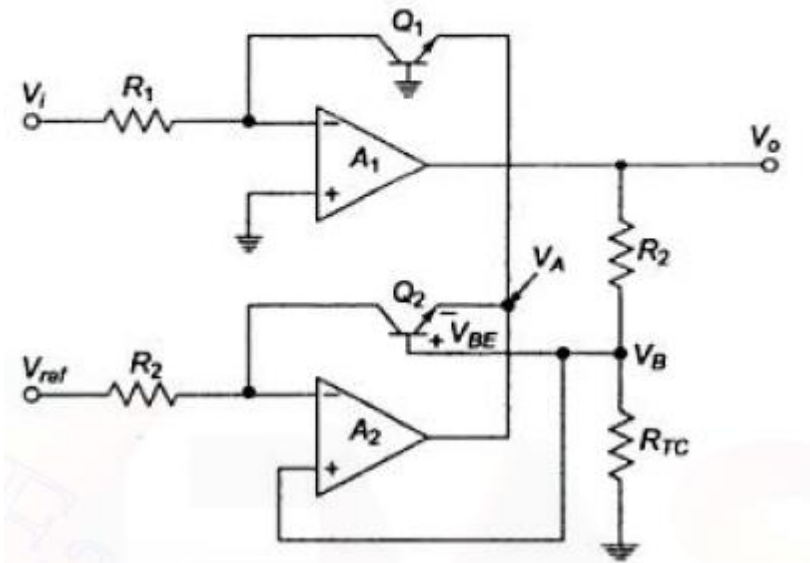


Fig.2.30 Logarithmic amplifier using two op amps

Where R_{TC} is a temperature-sensitive resistance with a positive coefficient of temperature (sensor) so that the slope of the equation becomes constant as the temperature changes.

2.12 Antilog Amplifier

A circuit to convert logarithmically encoded signal to real signals. Transistor in inverting input converts input voltage into logarithmically varying currents

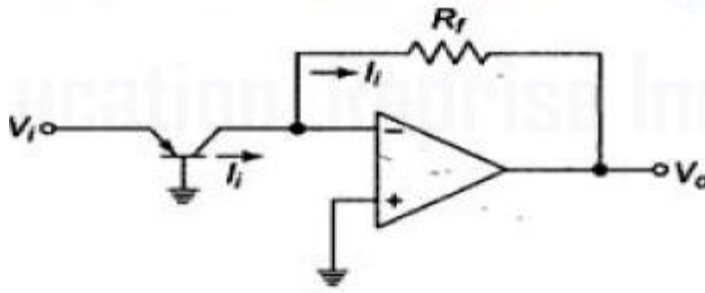


Fig. 2.31 Antilog amplifier

$$I_i = I_c = I_s \left(e^{\frac{\eta V_{BE}}{kT}} \right) \quad \text{and} \quad V_0 = R_f I_s \left(e^{\frac{\eta V_{BE}}{kT}} \right)$$

The circuit is shown in figure below. The input V_i for the antilog-amp is fed into the temperature compensating voltage divider R_2 and R_{TC} and then to the base of Q_2 . The output of A_2 is fed back to R_1 at the inverting input of op amp A_1 . The non-inverting inputs are grounded

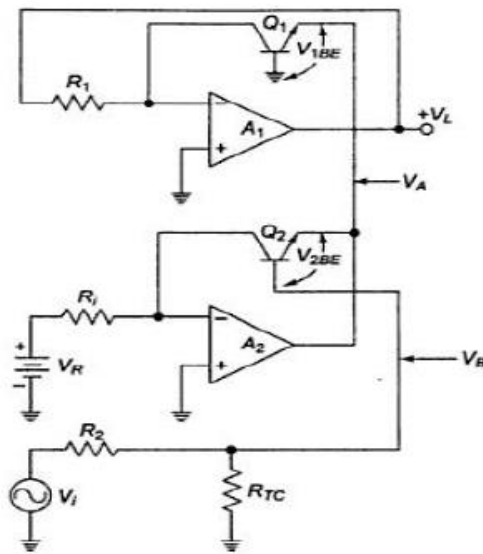


Fig 2.32 Antilog amplifier

$$V_{1BE} = \frac{kT}{q} \ln\left[\frac{V_L}{R_1 I_S}\right] \quad \text{and} \quad V_{2BE} = \frac{kT}{q} \ln\left[\frac{V_B}{R_1 I_S}\right] \quad \text{and} \quad V_A = -V_{1BE} \quad \text{and} \quad V_B = \frac{R_{TC}}{R_2 + R_{TC}} V_i$$

$$V_{Q2E} = V_B + V_{2BE} = \frac{R_{TC}}{R_2 + R_{TC}} V_i - \frac{kT}{q} \ln\left[\frac{V_B}{R_1 I_S}\right]$$

$$V_{Q2E} = V_A$$

Therefore,

$$-\frac{kT}{q} \ln\left(\frac{V_L}{R_1 I_S}\right) = \frac{R_{TC}}{R_2 + R_{TC}} V_i + \frac{kT}{q} \ln\left(\frac{V_B}{R_1 I_S}\right)$$

Rearranging, we get

$$\begin{aligned} \frac{R_{TC}}{R_2 + R_{TC}} V_i &= -\frac{kT}{q} \ln\left(\frac{V_L}{R_1 I_S}\right) - \frac{kT}{q} \ln\left(\frac{V_B}{R_1 I_S}\right) \\ &= -\frac{kT}{q} \ln\left(\frac{V_L}{V_B}\right) \end{aligned}$$

We know that $\log_{10} x = 0.4343 \ln x$.

$$\text{Therefore,} \quad -0.4343 \left(\frac{q}{kT}\right) \left(\frac{R_{TC}}{R_2 + R_{TC}}\right) V_i = 0.4343 \ln\left(\frac{V_L}{V_B}\right)$$

$$-0.4343 \left(\frac{q}{kT}\right) \left(\frac{R_{TC}}{R_2 + R_{TC}}\right) V_i = \log_{10}\left(\frac{V_L}{V_B}\right)$$

$$-KV_i = \log\left(\frac{V_L}{V_B}\right)$$

$$K = 0.4343 \left(\frac{q}{kT}\right) \left(\frac{R_{TC}}{R_2 + R_{TC}}\right)$$

$$V_L = V_B 10^{-KV_i}$$

The output V_0 of the antilog- amp is fed back to the inverting input of A1 through the resistor R_1 . Hence an increase of input by one volt causes the output to decrease by a decade.

Analog Multipliers:

A multiplier produces an output V_0 which is proportional to the product of two inputs V_x and V_y . $V_0 = K V_x V_y$ where K is the scaling factor = (1/10) V⁻¹.

There are various methods available for performing analog multiplication. Four of such techniques, namely,

1. Logarithmic summing technique
2. Pulse height/width modulation Technique
3. Variable trans conductance Technique
4. Multiplication using Gilbert cell and
5. Multiplication using variable trans conductance technique.

An actual multiplier has its output voltage V_0 defined by

$$V_0 = \frac{(V_x + \phi_x)(V_y + \phi_y)}{10(1 + \epsilon)} + \phi_0$$

where ϕ_x and ϕ_y are the offsets associated with signals V_x and V_y , ϵ is the error signal associated with K and ϕ_0 is the offset voltage of the multiplier output.

Terminologies associated voltage of the multiplier characteristics:

✓ Accuracy:

This specifies the derivation of the actual output from the ideal output, for any combination of X and Y inputs falling within the permissible operating range of the multiplier.

✓ Linearity:

This defines the accuracy of the multiplier. The Linearity Error can be defined as the maximum absolute derivation of the error surface. This linearity error imposes a lower limit on the multiplier accuracy.

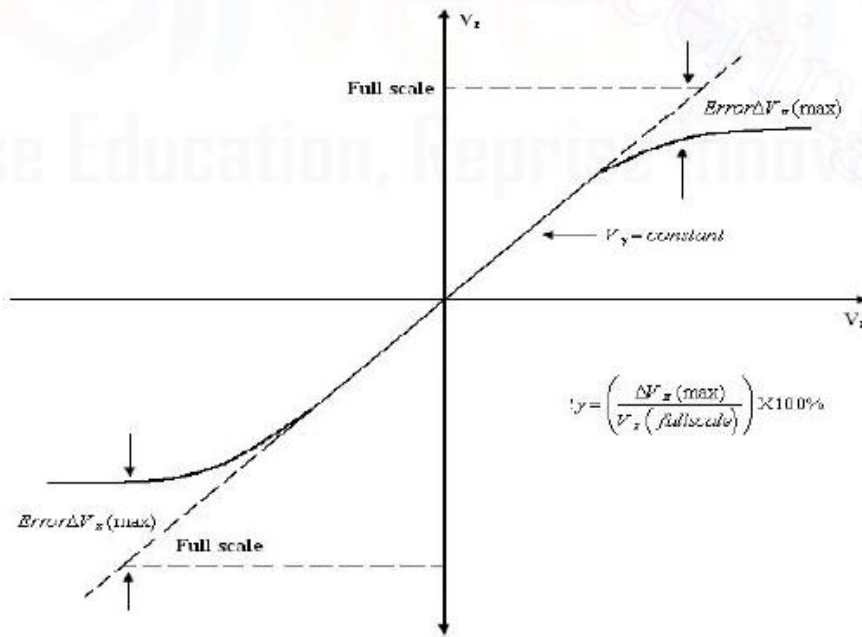


Fig.3.1 Linearity of the multiplier

The figure shows the response of the output as a function of one input voltage V_x when the other V_y is assumed constant. It represents the maximum percentage derivation from the ideal straight line output. An error surface is formed by plotting the output for different combinations of X and Y inputs.

✓ Square law accuracy:

The Square – law curve is obtained with the X and Y inputs connected together and applied with the same input signal. The maximum derivation of the output voltage from an ideal square –law curve expresses the squaring mode accuracy.

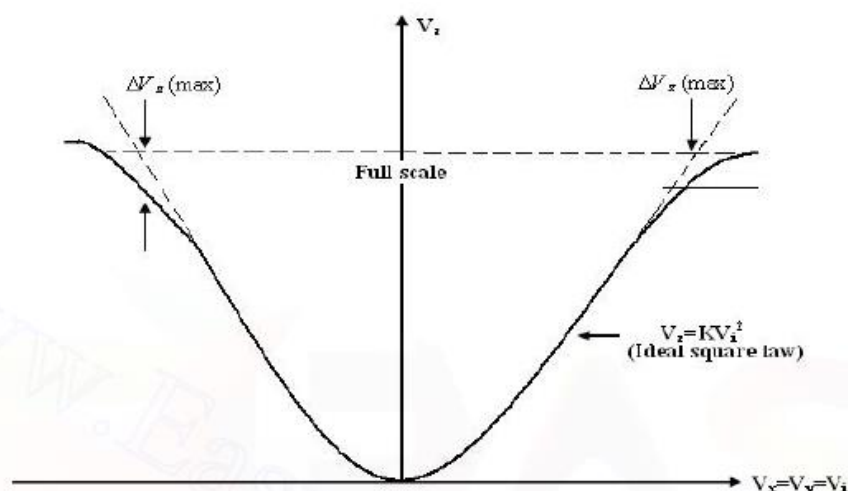


Fig. 3.2 squaring mode accuracy

✓ Bandwidth:

The Bandwidth indicates the operating capability of an analog multiplier at higher frequency values. Small signal 3 dB bandwidth defines the frequency f_0 at which the output reduces by 3dB from its low frequency value for a constant input voltage. This is identified individually for the X and Y input channels normally.

The transconductance bandwidth represents the frequency at which the transconductance of the multiplier drops by 3dB of its low frequency value. This characteristic defines the application frequency ranges when used for phase detection or AM detection.

✓ Quadrant:

The quadrant defines the applicability of the circuit for bipolar signals at its inputs. First – quadrant device accepts only positive input signals, the two quadrant device accepts one bipolar signal and one unipolar signal and the four quadrant device accepts two bipolar signals.

✓ Logarithmic summing Technique:

This technique uses the relationship $\ln V_x + \ln V_y = \ln(V_x V_y)$ As shown in figure the input voltages V_x and V_y are converted to their logarithmic equivalent, which are then added together by a summer. An antilogarithmic converter produces the output voltage of the summer.

The output is given by,

$$V_z = \ln^{-1} (\ln(V_x V_y)) = V_x V_y .$$

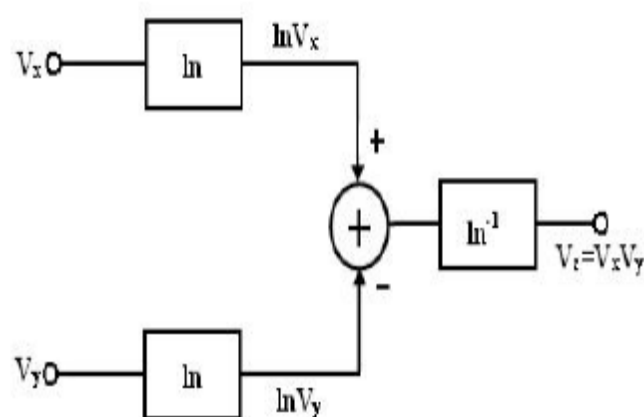


Fig. 3.3 logarithmic summing method

The relationship between I_0 and V_{BE} of the transistor is given by $I_C = I_0 e^{(V_{BE} / V_T)}$. It is found that the transistor follows the relationship very accurately in the range of 10nA to 100mA. Logarithmic multiplier has low accuracy and high temperature instability. This method is applicable only to positive values of V_x and V_y .

Limitation: this type of multiplier is restricted to one quadrant operation only.

✓ Pulse Height/ Width Modulation Technique:

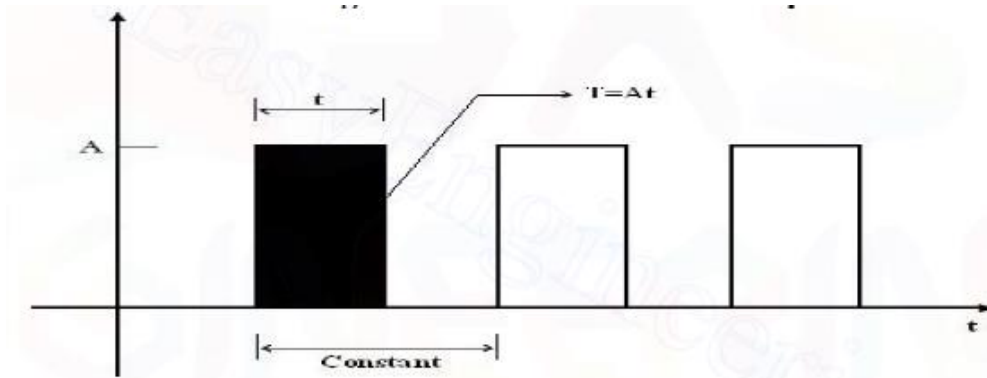


Fig.3.4 Pulse Height/ Width Modulation Technique

In this method, the pulse width of a pulse train is made proportional to one input voltage and the pulse amplitude is made proportional to the second input voltage. Therefore, $V_x = K_x A$, $V_y = K_y t$, and $V_z = K_z T$ where K_x , K_y , K_z are scaling factors. In figure A is the amplitude of the pulse, t is the pulse width and T is the area of the pulse. Therefore,

$$V_z = K_z T = \frac{V_x V_y}{k_x k_y}$$

The modulated pulse train is passed through an integrated circuit. Therefore, the input of the integrator is proportional to the area of pulse, which in turn is proportional to the product of two input voltages.

Comparator

A comparator compares a signal voltage on one input of an op-amp with a known voltage called a reference voltage on the other input. Comparators are used in circuits such as,

- ✓ Digital Interfacing
- ✓ Schmitt Trigger
- ✓ Discriminator
- ✓ Voltage level detector and oscillators

2.13.1 Non-inverting Comparator:

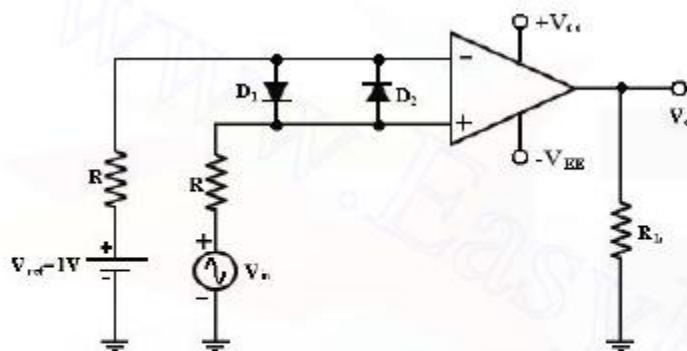


Fig. 2.33 non-inverting comparator circuit

A fixed reference voltage V_{ref} of 1 V is applied to the negative terminal and time varying signal voltage V_{in} is applied to the positive terminal.

When V_{in} is less than V_{ref} the output becomes V_0 at $-V_{sat}$

[$V_{in} < V_{ref} \Rightarrow V_0 (-V_{sat})$].

When V_{in} is greater than V_{ref} , the (+) input becomes positive, the V_0 goes to $+V_{sat}$.

[$V_{in} > V_{ref} \Rightarrow V_0 (+V_{sat})$].

Thus the V_0 changes from one saturation level to another.

The diodes D_1 and D_2 protect the op-amp from damage due to the excessive input voltage V_{in} . Because of these diodes, the difference input voltage V_{id} of the op-amp diodes are called clamp diodes.

The resistance R in series with V_{in} is used to limit the current through D_1 and D_2 . To reduce offset problems, a resistance $R_{comp} = R$ is connected between the (-ve) input and V_{ref} .

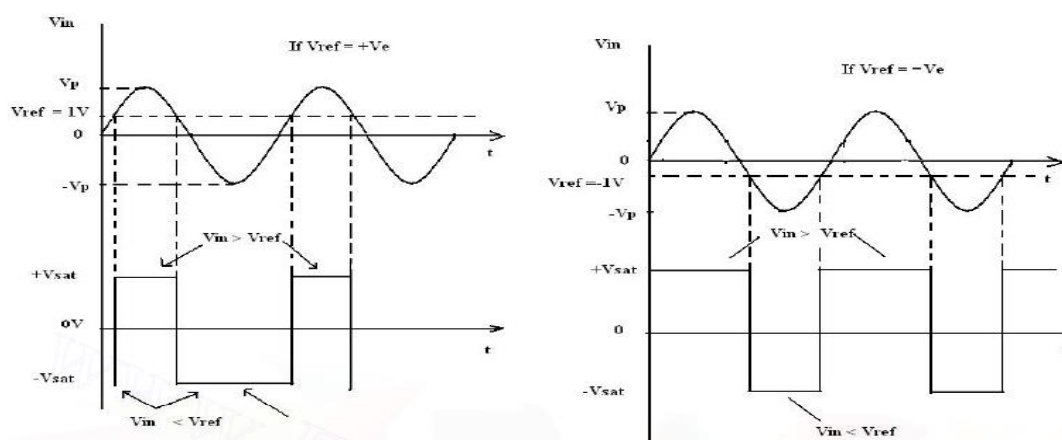


Fig. 2.34 Input and Output Waveforms of non-inverting comparator

2.13.2 Inverting Comparator:

This fig shows an inverting comparator in which the reference voltage V_{ref} is applied to the (+) input terminal and V_{in} is applied to the (-) input terminal.

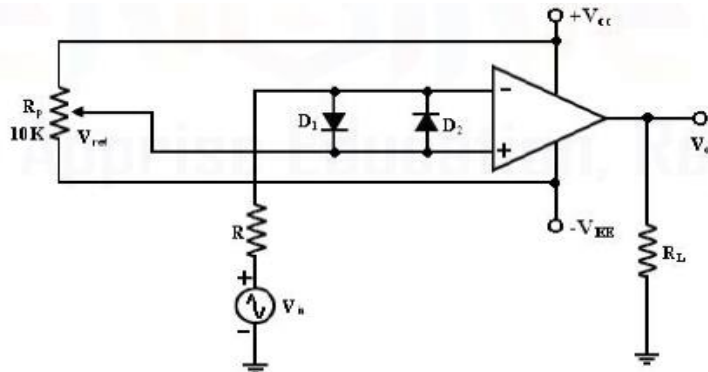


Fig. 2.35 Inverting comparator circuit

In this circuit V_{ref} is obtained by using a 10K potentiometer that forms a voltage divider with DC supply volt $+V_{cc}$ and $-V_{EE}$ and the wiper connected to the input. As the wiper is moved towards $+V_{cc}$, V_{ref} becomes more positive. Thus a V_{ref} of a desired amplitude and polarity can be got by simply adjusting the 10k potentiometer.

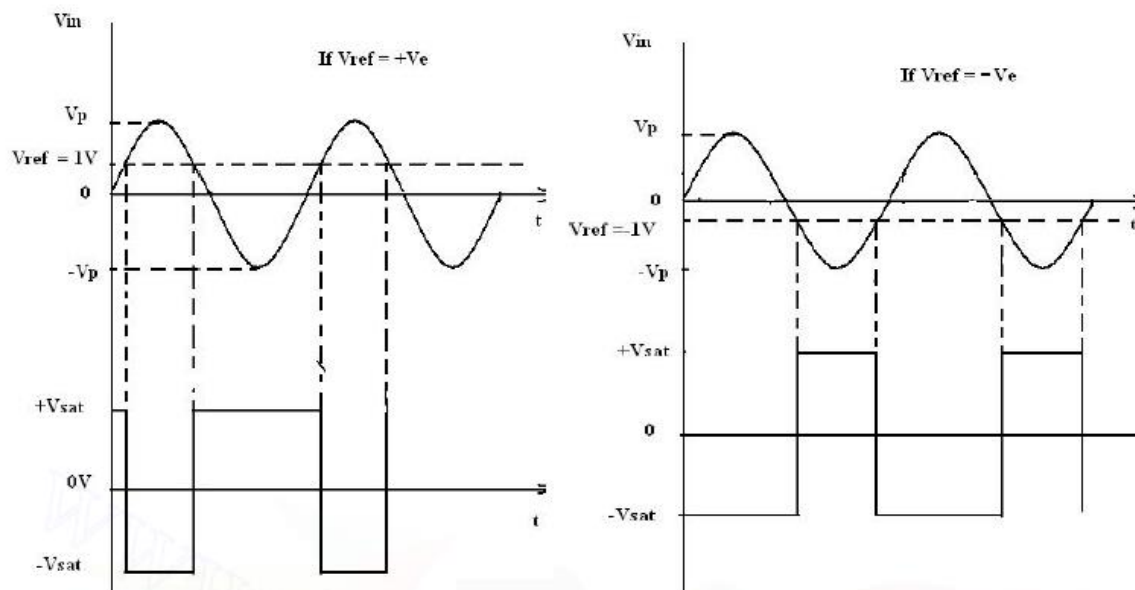


Fig. 2.36 Input and Output Waveforms of non-inverting comparator

Applications:

- ✓ Zero Crossing Detector: [Sine wave to Square wave converter]

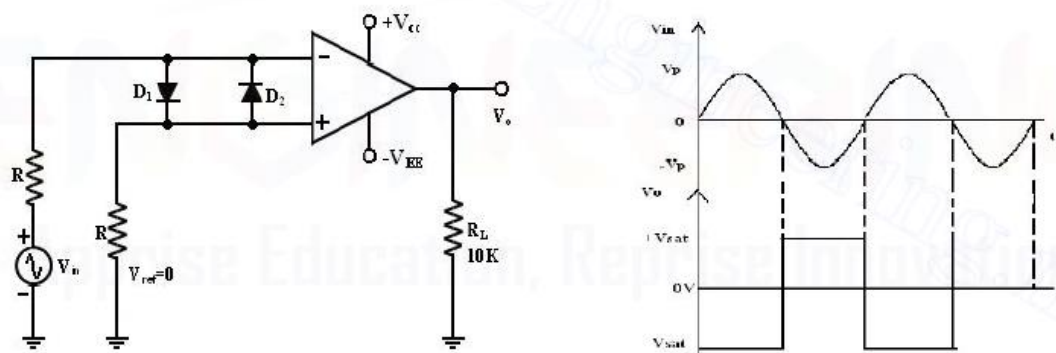


Fig. 2.37 Zero crossing detector circuit and input-output waveforms

One of the applications of comparator is the zero crossing detector or —sine wave to Square wave Converter. The basic comparator can be used as a zero crossing detector by setting V_{ref} is set to Zero. This Fig shows when in what direction an input signal V_{in} crosses zero volts. (i.e.) the o/p V_0 is driven into negative saturation when the input the signal V_{in} passes through zero in positive direction. Similarly, when V_{in} passes through Zero in negative direction the output V_0 switches and saturates positively.

- ✓ Drawbacks of Zero- crossing detector:

In some applications, the input V_{in} may be a slowly changing waveform, (i.e) a low frequency signal. It will take V_{in} more time to cross 0V, therefore V_0 may not switch quickly from one

saturation voltage to the other. Because of the noise at the op-amp's input terminals the output V_0 may fluctuate between 2 saturations voltages $+V_{sat}$ and $-V_{sat}$. Both of these problems can be cured with the use of regenerative or positive feedback that cause the output V_0 to change faster and eliminate any false output transitions due to noise signals at the input Inverting comparator with positive feedback. This is known as Schmitt Trigger.